

CSE 345: Digital Logic Design

Section: 1, Spring 2020

Project

Submitted by:

Group: 9

Group Members:

AMIT ROY	2017-3-60-021
SIRAJUM MARIA MUNA	2017-3-60-020
SHEKHOR CHANDRA SAHA	2017-3-60-025
MD NABID HOSSAIN	2017-3-60-059

Submitted to:

Musharrat Khan

Senior Lecturer, Dept. of CSE


East West University

Date of Submission:09-05-2020

Question 1:

Draw the block diagram, truth table, equation and logic diagram of a 2-to-4 lines decoder with active- LOW outputs and active-LOW enable input.

Block diagram:

 

Block Diagram

Truth table:

Inputs			Outputs			
E	A_0	A_1	O_3	O_2	O_1	O_0
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

Equation:


$$O_0 = E + A_1 + A_0 = (E' A_1' A_0')'$$

$$O_1 = E + A_1 + A_0' = (E' A_1' A_0)'$$

$$O_2 = E + A_1' + A_0 = (E' A_1 A_0')'$$

$$O_3 = E + A_1' + A_0' = (E' A_1 A_0)'$$


Logic diagram:

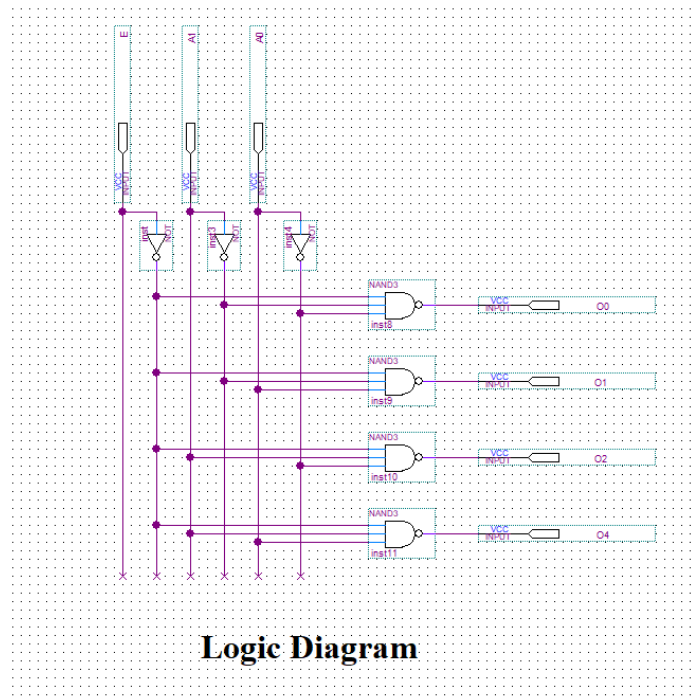

Question 2:

Draw the block diagram, truth table, equation and logic diagram of a 3-to-8-lines decoder with active-LOW outputs.

Block diagram:

 

Block Diagram

Truth table:

Inputs			outputs							
A_2	A_1	A_0	O_7	O_6	O_5	O_4	O_3	O_2	O_1	O_0
0	0	0	1	1	1	1	1	1	1	0
0	0	1	1	1	1	1	1	1	0	1
0	1	0	1	1	1	1	1	0	1	1
0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	1	1	0	1	1	1	1
1	0	1	1	1	0	1	1	1	1	1
1	1	0	1	0	1	1	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1

Equation:

$$O_0=A_2+A_1+A_0=(A_2'A_1'A_0')'$$

$$O_1 = A_2 + A_1 + A_0 \quad ' = (A_2' A_1' A_0)'$$

$$O_2 = A_2 + A_1' + A_0 = (A_2' A_1 A_0')'$$

$$O_3 = A_2 + A_1' + A_0' = (A_2' A_1 A_0)'$$


$$O_4=A_2'+A_1+A_0=(A_2A_1'A_0')'$$

$$O_5 = A_2' + A_1 + A_0' = (A_2 A_1' A_0)'$$

$$O_6 = A_2' + A_1' + A_0 = (A_2 A_1 A_0')'$$

$$O_7=A_2'+A_1'+A_0'=(A_2A_1A_0)'$$

Logic Diagram:

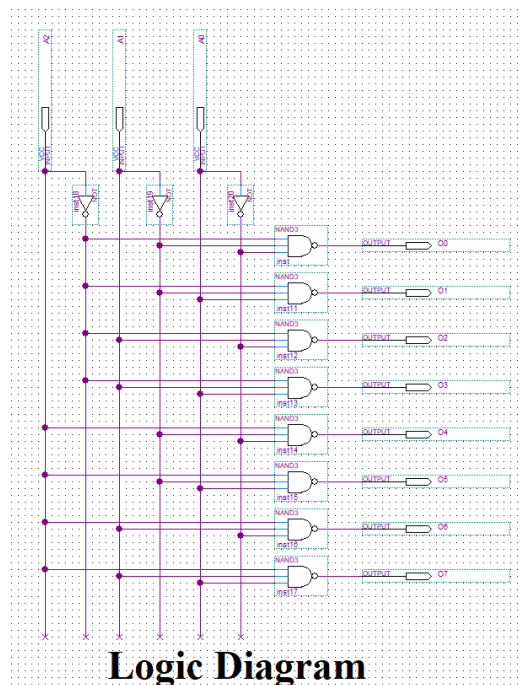


Question 3:

Write Structural Verilog code for logic diagram for 2-to-4-lines decoder with active-LOW outputs and active-LOW enable input and simulate it using Quartus II software.

Structural Verilog code:

```
module ques3(input E,A1,A0,output o0,o1,o2,o3);
nand (o0,~E,~A1,~A0),
(o1,~E,~A1,A0),
(o2,~E,A1,~A0),
(o3,~E,A1,A0);
Endmodule
```

Simulation:

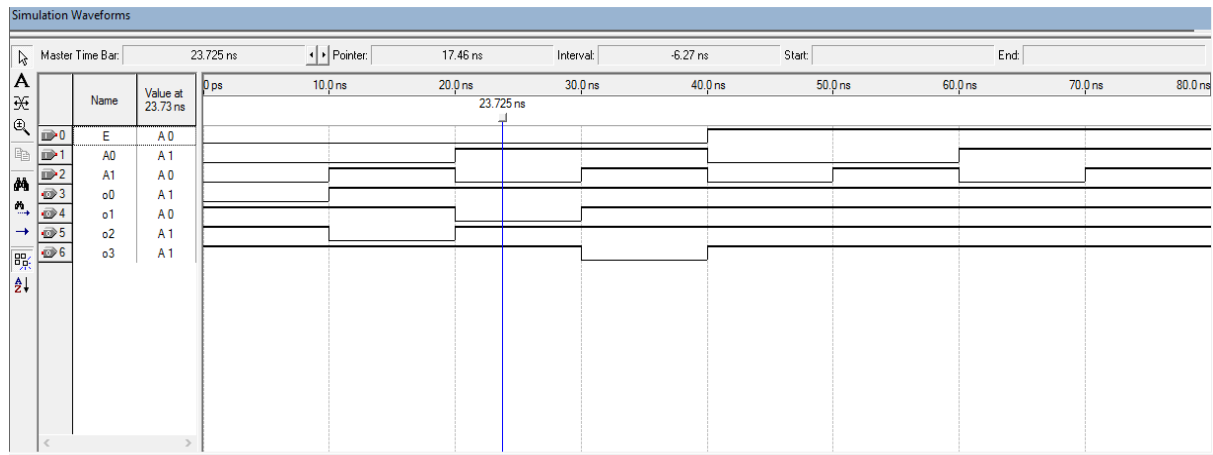

Question 4:

Write Behavioral Verilog code for 3-to-8-lines decoder with active-LOW outputs and simulate it using Quartus II software.

Behavioral verilog code:

Procedural model:

```
Module3by8decoder( input A2, A1, A0, output reg o0, o1, o2, o3, o4, o5, o6, o7);
```

```
always@( A2, A1,A0) begin
```

```
case( {A2, A1, A0})
```

3'b 000 : o0=0;

3'b 001 :o1=0;

3'b 010: o2=0;

3'b 011: o3=0;

3'b 100: o4=0;

3'b 101: o5=0;

3'b 110: o6=0;

3'b 111: o7=0;

End

Endcase

Continuous assign statement:

module 3by8decoderassign(input A2, A1, A0, output o0, o1, o2, o3, o4, o5, o6, o7);

assign o0=(~A2 & ~A1 & ~A0);

assign o1=(~A2 & ~A1 & A0);

assign o2=(~A2 & A1 & ~A0);

assign o3=(~A2 & A1 & A0);

assign o4=(A2 & ~A1 & ~A0);

assign o5=(A2 & ~A1 & A0);

assign o6=(A2 & A1 & ~ A0);

assign o7=(A2 & A1 & A0);

endmodule

Simulation:

